

Date
21/9/15

1

SPRIN

UNIT - VI

- V - I) Objectives of facts controllers in a PS n/w
- II - 2) Explain about midpoint regulation
- III - 3) Explain about objectives of shunt controller
- IV - 4) Explain about UPFC compensation

Shunt compensation

↓ Objectives of shunt compensation

Static VAR compensators < TCR + Tm
Comparison between SVC & STATCOM

* * * * power transfer

power oscillation damping

Improvement of SSSL & TSSL

* Static shunt compensation:-

A shunt reactor (or) capacitor is used for shunt compensation.

Objectives:-


- i To improve v/g profile.
- ii To increase power transfer.
- iii To improve steady state & transient state stability.
- iv To improve voltage stability on radial lines.
- v To control reactive power overlines in a large system to reduce power losses.

Methods of controllable VAR Generation

* Midpoint v/g regulation (MPVR):-

Advantages:-

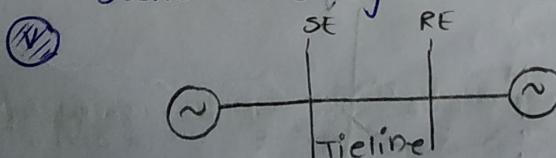- i Better v/g profile.
- ii Increased power transfer.
- iii To damp power oscillations.
- iv Increase in transient state stability & steady state stability limits.



SE - Sending End

RE - Receiving End


Date
22/9/15

① Better v/g profile:-

IV - T110U

Improvement of v/g - reactor power transfer capacity

②

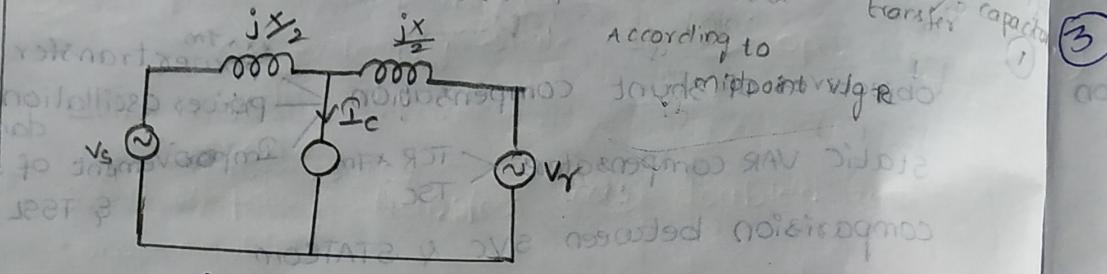

According to


(Resistance is neglected)

The phasor diagram without compensation is shown in figure (a) reactor mode A

$$\text{let } |V_s| = |V_g| = V$$

where

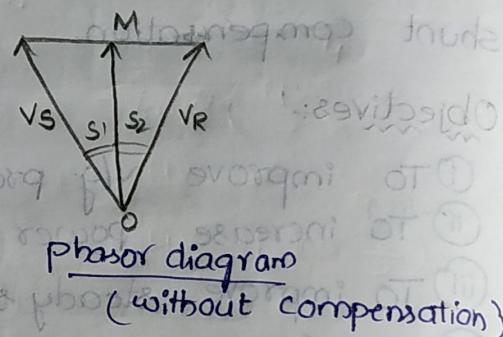OM gives the minimum v/g on the line at the midpoint.



Let a shunt compensator be located at midpoint & is so controlled that the v/g there is maintained constant at $|V_{st}| = |V_g| = V$.



Reactor is used as compensating element in midpoint v/g regulation.

ΔOSC and ΔORC

are 180° less & concurrent.

minimum v/g occurs at $\frac{1}{4}$ th & $\frac{3}{4}$ th of the line

i.e. OM_2 & OM_3 as shown in fig.

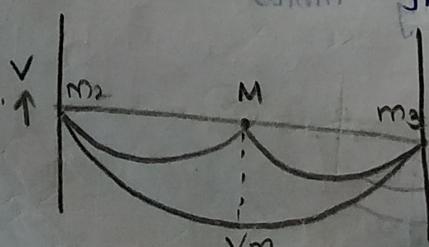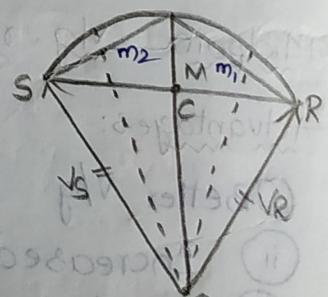

Without shunt compensator
Flat v/g profile with shunt compensator

OM_2 & OM_3 are greater than minimum v/g V_m without shunt compensator.



Flat v/g profile (or) better v/g profile is obtained using shunt compensator.

3

Imp

ii)

Improvement of power transfer (SSSL)

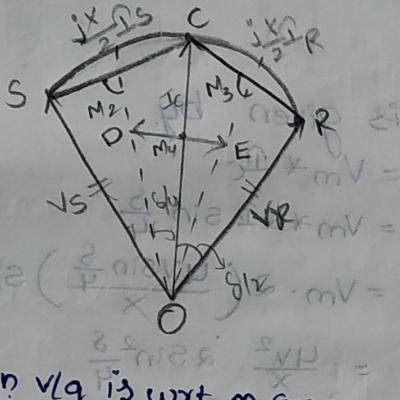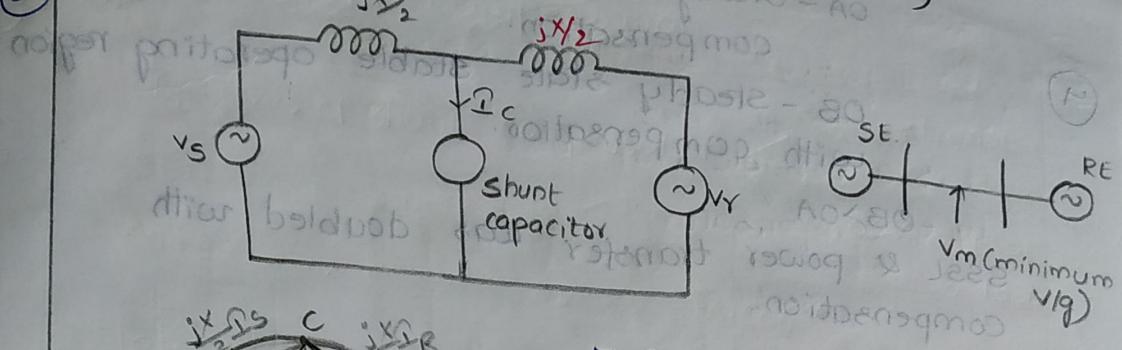

Min V_{lg} is wrt m_2 on
M₃ so the angles
shifted from S to

For power transfer capacitor is used as compensating element I_c loads V_m by 90° due to capacitor as compensating device Δ^{1es} osc & ORC are isosceles & concurrent.

$$P = P_s = V_s I_s \cos \frac{\delta}{4}$$

(same everywhere)

fixed pt. load & static load part to this working
substituting this value in

$$P = V_s I_s \cos \frac{\delta}{4} \text{ we get}$$

$$P = \frac{4V^2}{X} \sin \frac{\delta}{4} \cos \frac{\delta}{4} = \frac{2V^2}{X} \sin \frac{\delta}{2}$$

$$\text{In } \Delta ODE = I_s = I_R = I$$


$$P = V I \cos \phi = \frac{V^2}{X} \sin \frac{\delta}{2}$$

M_4 is a mid point, $\frac{I_c}{2} = I \sin \frac{\delta}{4}$

Necessary for compensation

$$I_c = 2I \sin \frac{\delta}{4}$$
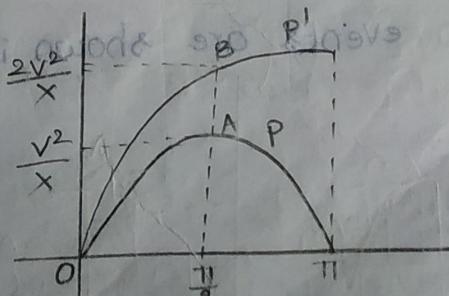
$$\text{In } \Delta OSC, \sin \frac{\delta}{2} = \frac{V_s}{X} = \frac{V}{X}$$



(1) OA - Steady state stability region without compensation.

(2) OB - steady state stable operating region with compensation.

$OB > OA$

SSSL & power transfer was doubled with compensation.

Rating of compensation is given by

$$= V_m * \frac{\Delta}{X}$$

V_m = minimum voltage that occurs at mid point

$$= V_m * 2 \Delta \sin \frac{\delta}{4}$$

$$= V_m * 2 \left(\frac{4V \sin \frac{\delta}{4}}{X} \right) \sin \frac{\delta}{4}$$

$$= \frac{4V^2}{X} \cdot 2 \sin^2 \frac{\delta}{4}$$

$$= \frac{4V^2}{X} \left(1 - \cos \frac{\delta}{2} \right)$$

or $\frac{2}{\mu} \text{ cos} \frac{\delta}{2} = 1 - \cos \frac{\delta}{2}$

* Improvement of transient state stability limit.

* TSSSL (Equal area criterion).

$$\frac{2}{\mu} \cos \frac{\delta}{2} = 1$$

Without midpoint voltage regulation, $P = \frac{V^2}{X} \sin \delta$ - ①

With midpoint voltage regulation, $P = \frac{2V^2}{X} \sin \frac{\delta}{2}$ - ②

$$\Delta = \frac{\Delta}{2} = \frac{\Delta}{2} = 300 \Delta$$

Let the system be operating with an initial power of P_0 .

Let an short circuit fault occur which makes power transfer zero. $P_0 = 0$


Let the fault be cleared after a delay time given by an δ_c .

These events are shown in the following

2 causes.

power angle curves

swing curve
TSSL

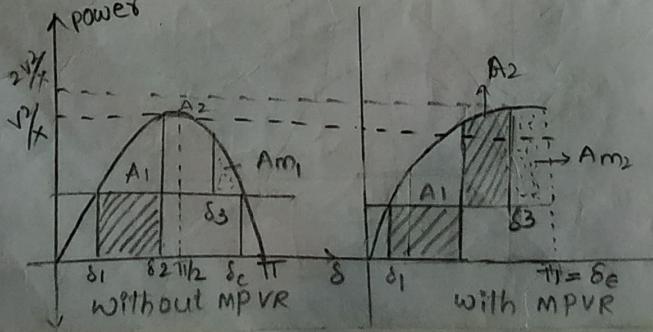

A₁ = accelerating area


A₂ = deaccelerating area

$A_{m2} > A_{m1}$

TSSL is improved

(5)

Date
20/11/15

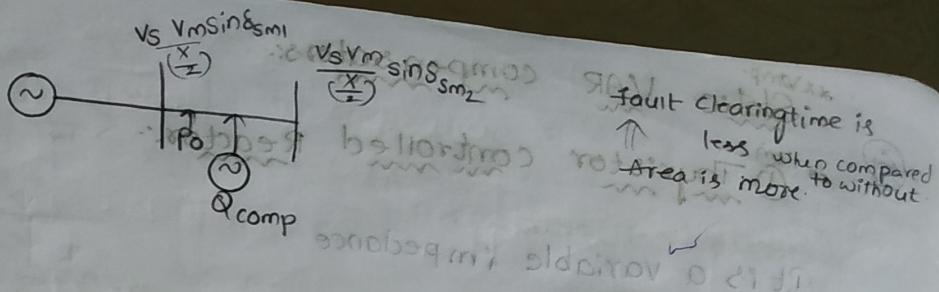

Power Oscillation damping:-


System is stable, $P_0 = P_i$



Due to disturbance let P' falls temporarily.

$P_0 < P_i \sim$ The machine accelerates, δ increases.
 $\frac{d\delta}{dt} > 0$, power increases.

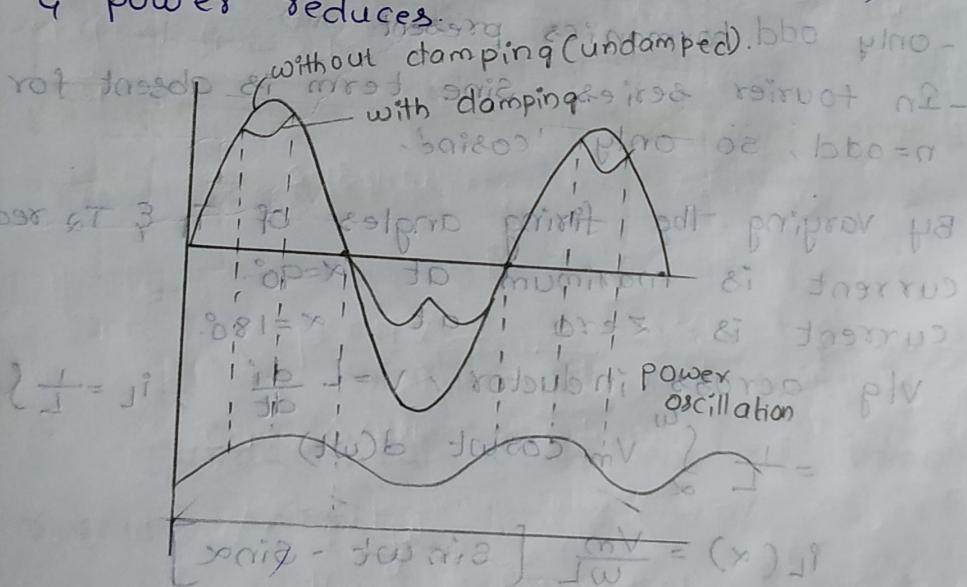$P_0 > P_i \sim$ The machine deaccelerates, δ decreases,
& power reduces.



$P_0 < P_i \rightarrow$ During accelerating period shunt compensator (reactor) absorb leading reactive power so that V_m increases & hence P_0 increases. This reduces the rate of δ & so the rate of increase of power.


$P_0 > P_i \rightarrow$ During deaccelerating period, shunt compensator (capacitor) absorbs lagging reactive power so V_m decrease & hence P_0 reduces like this oscillation of power & δ are damped.

(6)

~~xx Vmp.~~
Static VAR compensators:

~~xx 14m~~
① Thyristor controlled Reactor: - $\frac{T_{CR}}{T_{SC}} < \frac{I_{mp}}{cap - force}$

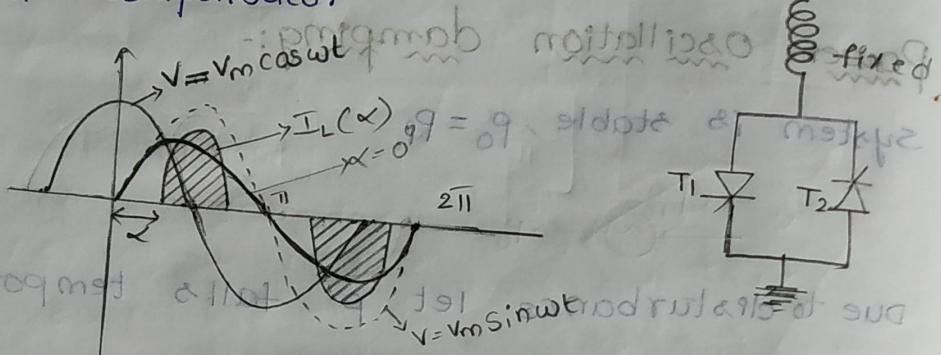It is a variable impedance type compensator.



$$V = V_m \sin(90^\circ - \omega t) \quad \text{lagging nature}$$

$$V = V_m \cos \omega t.$$

- only odd harmonics present (AC) $\Rightarrow \omega_0 \beta$
- In fourier series Sine term is absent for $n=odd$, so only 'cosine'.

By varying the firing angles of T_1 & T_2 reactor current is maximum at $\alpha = 90^\circ$.
 Current is zero at $\alpha = 180^\circ$.

Vlg across inductor, $V = L \frac{di}{dt}$, $i_L = \frac{1}{L} \int v dt$.

$$= \frac{1}{L} \int_{\alpha}^{\omega} V_m \cos \omega t d(\omega t)$$

$$i_L(\alpha) = \frac{V_m}{\omega L} [\sin \omega t - \sin \alpha]$$

$$\begin{aligned} ① b_1 &= \frac{2}{\pi} \int_0^{\pi} f(t) \sin \omega t d(\omega t) \\ &= \frac{2}{\pi} \int_{\alpha}^{\pi} \frac{V_m}{\omega L} (\sin \omega t - \sin \alpha) \sin \omega t d\omega t \\ &= \frac{2V_m}{\pi \omega L} \int_{\alpha}^{\pi} (\sin^2 \omega t - \sin \alpha \sin \omega t) d\omega t \\ &= \frac{2V_m}{\pi \omega L} \int_{\alpha}^{\pi} \left(\frac{1 - \cos 2\omega t}{2} - \frac{\sin \alpha \sin \omega t}{2} \right) d\omega t \\ &= \frac{2V_m}{\pi \omega L} \left(\frac{1}{2}(0) \frac{\pi - \alpha}{2} - \frac{(\sin \alpha)}{4} \right) - \sin \alpha \cos \alpha \end{aligned}$$

$$= \frac{2V_m}{\pi \omega L} \left[\frac{1}{2}(\pi - \alpha - \alpha) - \left(\frac{\sin \frac{\alpha(\pi-\alpha)}{4}}{4} - \frac{\sin \frac{\alpha}{4}}{4} \right) \right] \\ = -\sin \alpha [-\cos(\pi - \alpha) + \cos \alpha]$$

$$= \frac{2V_m}{\pi \omega L} \left[\frac{1}{2}(\pi - 2\alpha) - \frac{\sin \frac{(2\pi - 2\alpha)}{4}}{4} + \frac{\sin \frac{2\alpha}{4}}{4} \right] \\ = -\sin \alpha (\cos \alpha + \cos \alpha)$$

$$b_1 = \frac{2V_m}{\pi \omega L} \left[\frac{\pi}{2} - \alpha - 2\sin \alpha \cos \alpha + \frac{2\sin 2\alpha}{4} \right]$$

$$= \frac{2V_m}{\pi \omega L} \left[\left(\frac{\pi - 2\alpha}{2} \right) - \sin 2\alpha + \frac{\sin 2\alpha}{2} \right]$$

$$= \frac{2V_m}{\pi \omega L} \left[\frac{\pi - 2\alpha}{2} - \frac{\sin 2\alpha}{2} \right]$$

$$b_1 = \frac{V_m}{\omega L} \left(1 - \frac{2\alpha}{\pi} - \frac{\sin 2\alpha}{\pi} \right)$$

By changing firing angle to control reactor current.

Reactor current



$$i_L = b_1 \sin \omega t$$

$$i_L(\alpha) = \frac{V_m}{\omega L} \left(1 - \frac{2\alpha}{\pi} - \frac{\sin 2\alpha}{\pi} \right) \sin \omega t$$

Fundamental component of harmonic reactor current.

$$I_Q = \text{quadrature current} = I_{LF}(\alpha) - I_C$$

$$Q_C = I_Q V = V [I_{LF} - I_C]$$

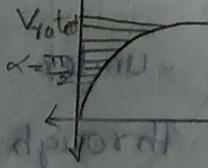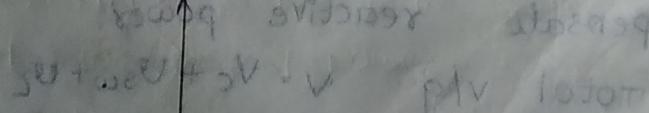


$$\frac{V_b}{I_b} \rightarrow V-Q \text{ characteristics}$$

(Impedance control by using current)

⑧

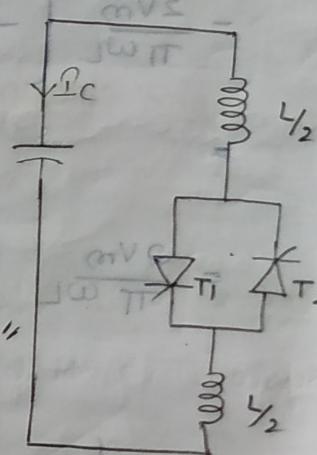FC-TCR provides compensation for both Inductive & Capacitive elements.



$$\begin{aligned} \Omega_C &= B_C V \\ \Omega_L &= B_L F(\omega) V \left(\frac{\omega}{\omega_0 - \Omega} \right)^{\frac{1}{2}} \end{aligned}$$

$$B_L F(\omega) = \frac{1}{\omega L} \left[1 - \frac{2\zeta}{\pi} - \frac{\sin \alpha}{\pi} \right]$$

$$B = \frac{1}{\lambda}$$



Thyristor switched reactor

$$\left[\frac{x_B}{\omega} + x_{C_R} \right] \frac{V_m}{\omega \pi} = id$$

26/9/15


* Thyristor switched capacitor (TSC)

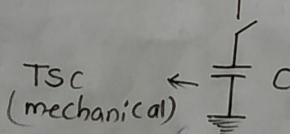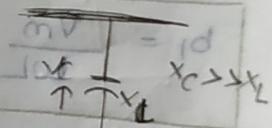Thyristor switching is faster than mechanical switching.



-capacitor 'C' will be either in the ckt or out of the ckt.

$$V = \frac{1}{C} \int idt.$$

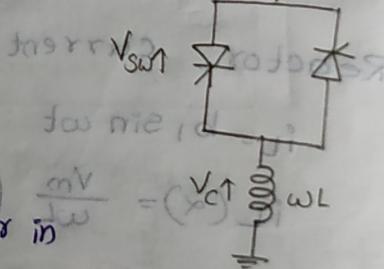

-TCR & TSC are used to overcome surges.

They provide over current protection.

Here λ_L is used to damp surges but not to compensate reactive power

$$\text{Total v/g } V = V_C + V_{SW} + V_L$$

T_1 & T_2 conducting under steady state conditions, the current through E is obtained as follows.

$$\text{Let } V = V_m \sin \omega t, q = C \frac{dv}{dt}$$

$$\text{Current through } C = \frac{V_m}{X_C - X_L} \cos \omega t \quad (\because X_C \gg X_L)$$

$$\text{IMPEDANCE base case} \Rightarrow \frac{V_m}{X_C \left[1 - \frac{X_L}{X_C} \right]} \cos \omega t$$

$$= \frac{V_m}{X_C \left[1 - \frac{1}{n^2} \right]} \cos \omega t$$

$$\therefore I = \frac{n^2}{n^2 - 1} \frac{V_m}{X_C} \cos \omega t \quad (\therefore \sqrt{\frac{X_C}{X_L}} = n)$$

V_g across the inductor L

$$V_L = L \frac{di}{dt}$$

$$V_L = L \left(\frac{n^2}{n^2 - 1} \frac{V_m}{X_C} \cos \omega t \right) \frac{d}{dt}$$

$$= L \frac{V_m}{X_C} \frac{n^2}{n^2 - 1} (-\sin \omega t) \omega$$

$$= -\omega L \frac{n^2}{n^2 - 1} \frac{V_m}{X_C} \sin \omega t$$

$$= -\left(\frac{X_L}{X_C}\right) \frac{n^2}{n^2 - 1} V_m \sin \omega t$$

$$= -\frac{n^2}{n^2 - 1} \cdot \frac{1}{n^2} V_m \sin \omega t$$

$$V_L = \frac{-1}{n^2 - 1} V_m \sin \omega t$$

$$Q_C = V I_C = \frac{V^2}{X_C}$$

For transient free operation
 $V = V_C$


Drawback:

1. Design parameter n must be designed where it is not required in case of TCR.
2. Cost of TSC is more than TCR.
3. Delta connection of 3 single phase TCR's eliminates Tripple harmonics.


due to charging and discharging of capacitor.

28/9/15

Comparison between SVC and STATCOM:

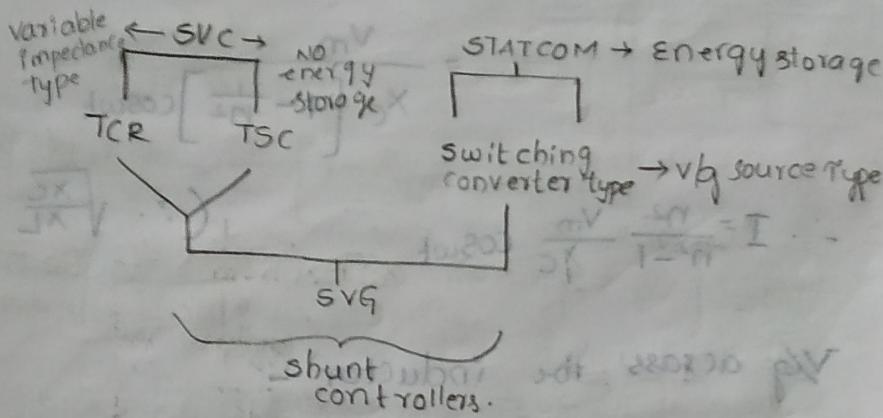


1) V-I characteristics:-

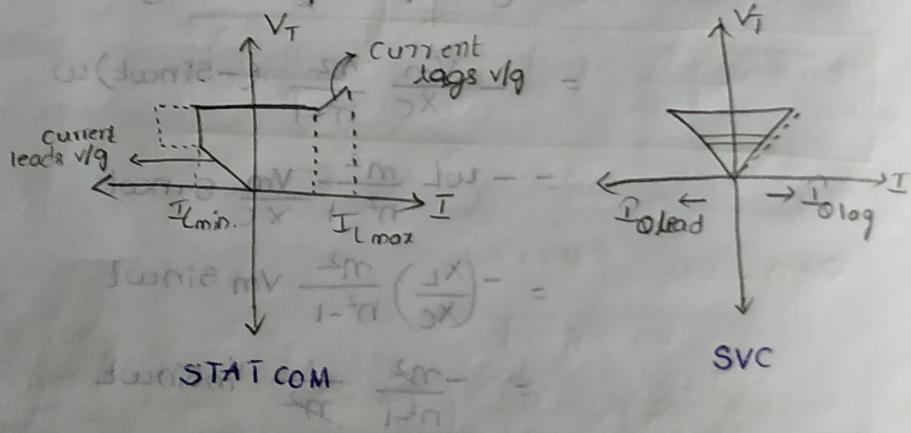

In STATCOM, max current will not reduce with v/g .


In SVC max current reduces linearly with the v/g drooping characteristics for SVC.

2) V-Q characteristics:

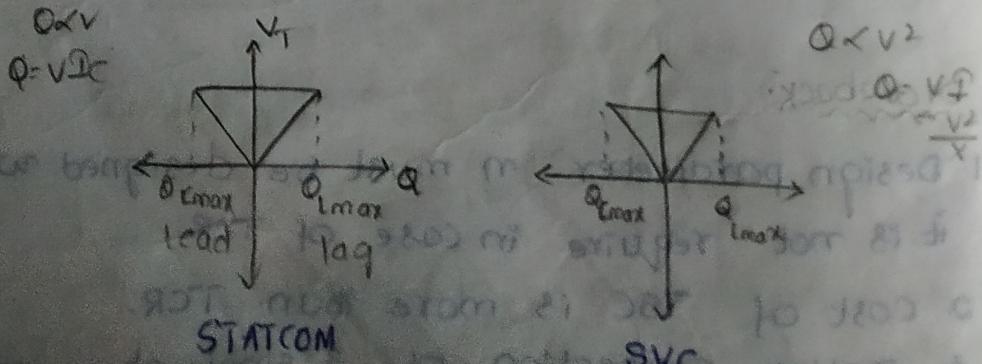


- linear characteristics in STATCOM and exponential characteristics in SVC.
- Reduction of V/g in results in reduction of Q in STATCOM

③ Transient stability enhancement:-

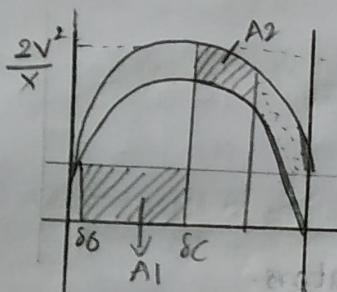

SVC

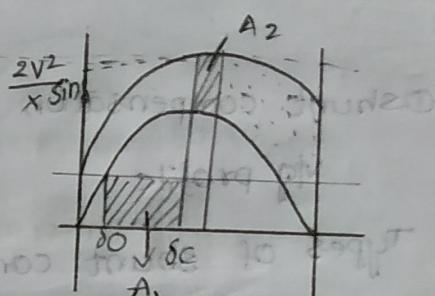

STATCOM

A₁ - Accelerating area
A₂ = Decelerating area

- Marginal area is more in STATCOM. S_c is more for SVC. After post fault the area not affected by fault is more in STATCOM & the area in SVC is less.
- power carrying capability for STATCOM is more.

④ Response time :- (ON OR OFF w.r.t fault condition)

TCR & TSC \rightarrow upto 2.5msec $\rightarrow \frac{1}{2}$ cycle

TCR \rightarrow upto 5msec \rightarrow 1 cycle

STATCOM - 200usec - 350usec (Fast response).

⑤ Operation with unbalanced v/g's.

STATCOM : O/p v/g will have negative sequence fundamental & a third harmonic v/g.

SVC : unbalanced v/g's, unequal compensating currents in lines.

⑥ Physical size:

(12)


STATCOM has only one capacitor occupies less space (30-90%) & low installation cost.

SVG requires bank of capacitors & reactors which are large in size & cost is more.

① Shunt compensation

Vg profile

Types of shunt compensators.

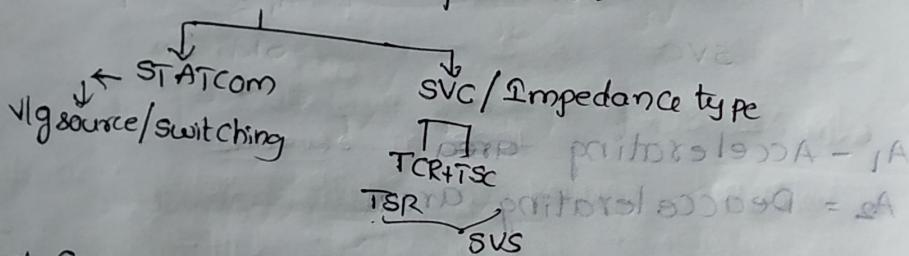

→ Compensation of STATCOM & SVC.

~~LCR & TCR & SVC & TSR~~

~~(STATCOM - 350 MVA - 1000 kV - 50 Hz)~~

~~• PIV requirement of STATCOM~~

~~• Switching time of STATCOM~~

~~• Power demand of STATCOM~~


~~• SVC requirement of STATCOM~~

①

UNIT - VII

Series Compensation

Objectives of series compensation

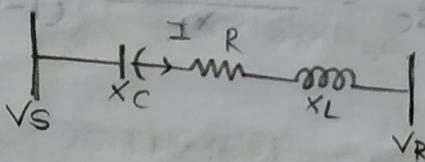
Net reactive drop $I(X_L - X_C)$ V_C is in phase opposition to V_R .

Objectives of series compensation:-

- ① Increase in Power Transfer.
- ② Improvement of steady state & transient state stabilities.
- ③ Improvement of v/g stability in radial lines.
- ④ power oscillation damping.

Improvement of power transfer:- on SSSL

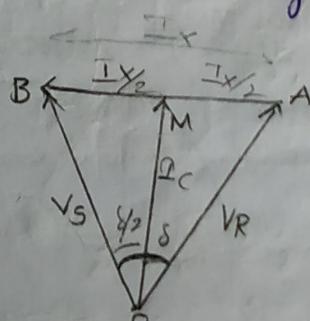The main objectives of series compensation is to decreased the overall effective series impedance from sending end to receiving end.



$$\text{let } X_C = k X_L$$

$$k = \frac{X_C}{X_L}$$

Degree of Series compensation
($0 \leq k \leq 1$)

$$\text{Then } X = (X_L - k X_L) = (1-k) X_L$$

$$\text{In } \triangle OAB, \tan \theta = \frac{V_r}{V_s} = \frac{1}{k}$$

$$\Rightarrow I = \frac{V_s}{X} \sin \frac{\theta}{2} \quad \text{--- (1)}$$

Power flow at sending end, $P_s = V I \cos \frac{\theta}{2} = V \cdot \frac{V_s}{X} \sin \frac{\theta}{2} \cos \frac{\theta}{2}$

$$k=0 \sim \text{uncompensated line} = \frac{V^2}{X} \sin^2 \theta = \frac{V^2}{(1-k)X_L} \sin^2 \theta \quad \text{--- (2)}$$

 $k < 1 \sim \text{compensated line}$

(2)

Reactive power, $Q_{SC} = \frac{\Omega^2}{X_C}$


$$= \frac{4V^2 \sin^2 \frac{\delta}{2}}{(X_L^2)(1-K)^2} K X_L$$

$$Q_{SC} = \frac{4V^2 \sin^2 \frac{\delta}{2}}{X_L} \cdot \frac{K}{(1-K)^2} - ③$$

$$P = \frac{V^2}{X} \sin \delta$$

$$P = \frac{2V^2}{X} \sin \delta$$

$$P = \frac{V^2}{(1-K)^2} \sin \delta$$

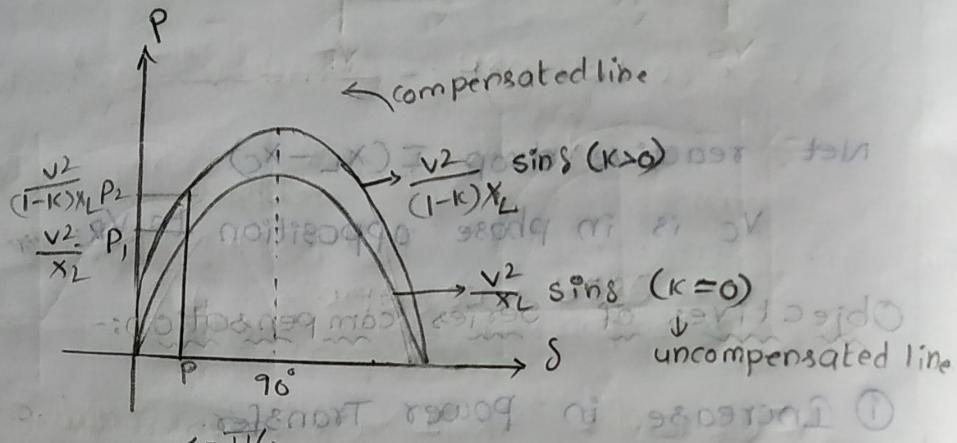
Increase in SSSL

- At any power angle δ power transfer is increased from $P_1 - P_2$

- Steady state stability is increased from $\frac{V^2}{XL}$ to $\frac{V^2}{(1-K)XL}$

- Enhancement of transient stability: +6% power amplitude

base point is at base point base point

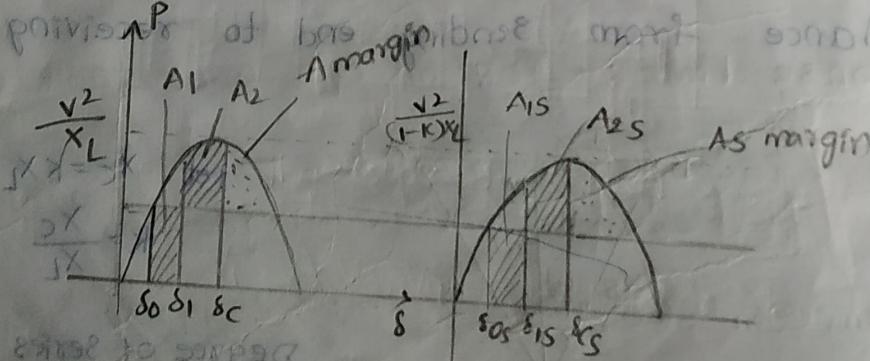


Margin area is more in case of series compensated line & hence transient stability is more.

Power oscillation damping:-

$$P_i - P_e = P_o$$

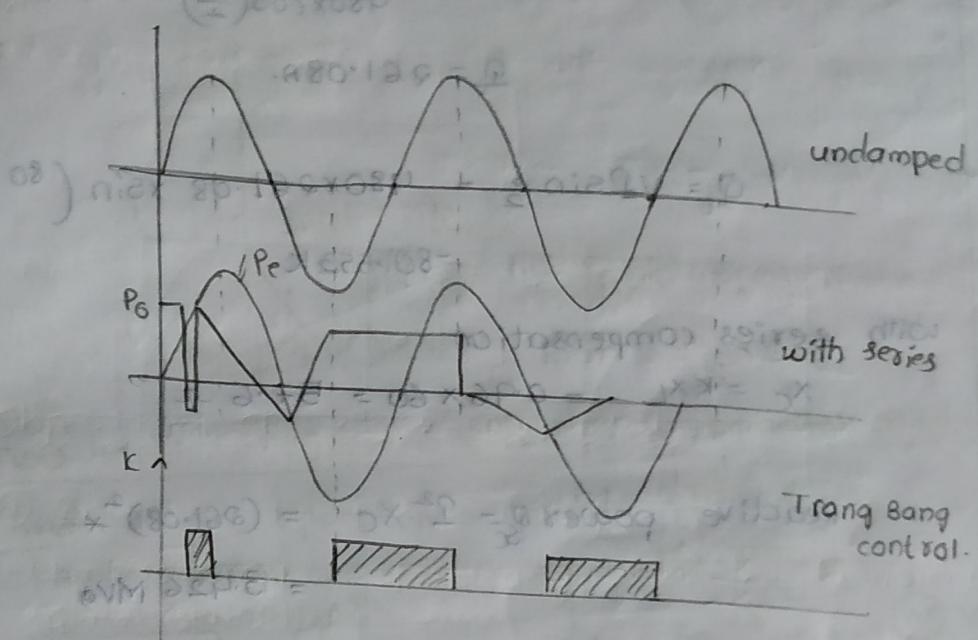(3)

By providing the series compensation during periods of acceleration, power oscillation can be damped.



① - For particulars of a series compensation transmission line with TCSC (Thyristor control series capacitor).

$$V = 480V, f = 60Hz, X_L = 60\Omega, P = 96kW, \delta = 80^\circ$$

The components of TSC are $C = 25\mu F$, $L = 40mH$

i) Find degree of compensation.

ii) Compensation of reactance.

iii) Reactive power flow in the line.

~~(a) ratio of load to total load~~

~~Given~~ $V = 480V, f = 60Hz, X_L = 60\Omega, P = 96kW$
 ~~$\delta = 80^\circ$~~

~~① $K = \frac{X_C}{X_L}$~~

$$X_C = 2\pi f C = 2\pi \times 60 \times 25 \times 10^{-6} = 9.427m\Omega$$

$$P = VI \cos \frac{\delta}{2}$$

No. of poles $P = \frac{V^2}{(1-K)X_L} \sin \delta$

$$96 \cdot \frac{1}{(1-K)} = \frac{V^2}{P \times X_L} \sin \delta = \frac{(480)^2}{96 \times 10^3 \times 60} \times \sin(80^\circ)$$

$$1-K = 0.0893$$

$$K = 0.96$$

$$(4) \quad P = V I \cos \frac{\delta}{2} \Rightarrow 96 \times 10^3 = 480 \times I \cos \left(\frac{80}{2} \right)$$

$$I = \frac{96 \times 10^3}{480 \times \cos(40)}$$

$$I = 261.08 \text{ A}$$

$$Q = V I \sin \frac{\delta}{2} = 480 \times 261.08 \times \sin(40)$$

$$= 80.553 \text{ kVAr}$$

with series compensation


$$X_C = K X_L = 0.96 \times 60 = 57.6 \Omega$$

$$\text{Reactive power } Q_{SC} = I^2 X_C = (261.08)^2 \times 57.6$$

$$= 3.926 \text{ MVA}$$

~~Variable Impedance type Series Compensators:~~
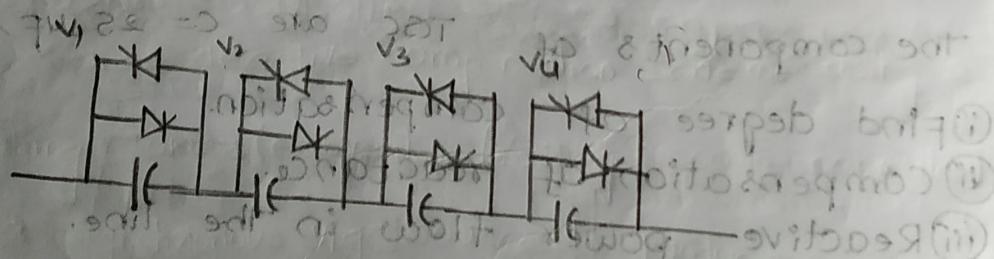
$$0.96 = 8, \omega L D = 9, \omega C D = 1, \omega H D = 1, V_0.8 H = V$$



Thyristor switched series capacitor (TSSC)


The degree of series compensation is controlled in a step like manner by increasing (or) decreasing the no. of series capacitors inserted.

A capacitor is inserted by turning off and it is bypassed by turning on the corresponding thyristor valve.

Time delay would be upto 1 cycle. This is called

$\frac{V_C}{I_{min}} = X_{TOTAL}$


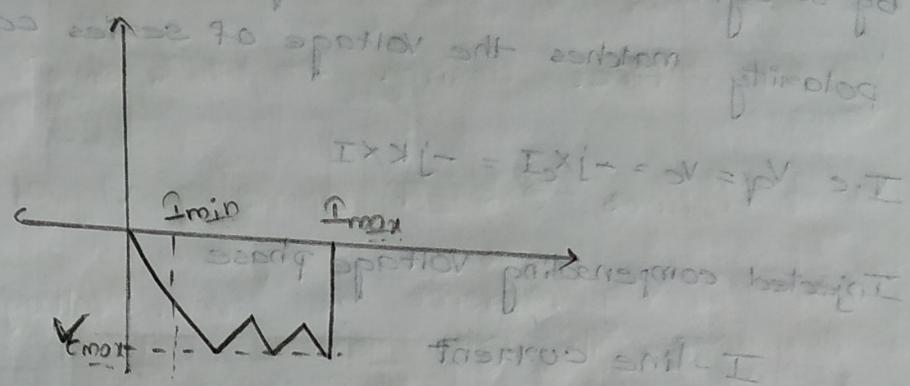
$V_{Cmax} = (X_{TOTAL}) \frac{I_{min}}{I_{max}}$



TWO Machine system with a series capacitor compensated

line (Basic operation of SSSC) $I \leftarrow V_b$ $\delta = \text{quadrature}$

with series capacitor V_s

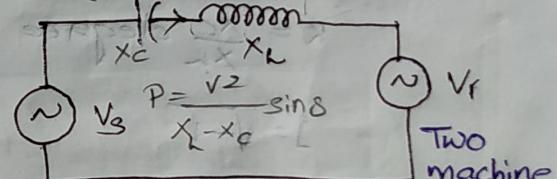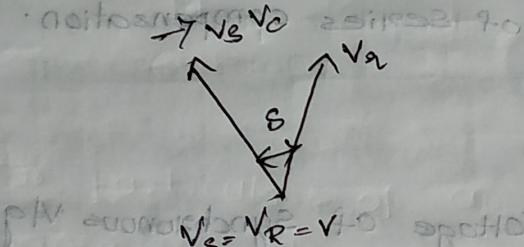


PN equation $V_s = V_R = V_2$ $\delta = 90^\circ$

(phasor diagram) \Rightarrow equivalent circuit diagram with series capacitor

the phasor diagram shows that at a given line power P_{av} , the series capacitor forces currents, the V_{lg} across the series capacitor forces the opposite polarity across the series line reactor to increase the magnitude of capacitor V_{lg} .

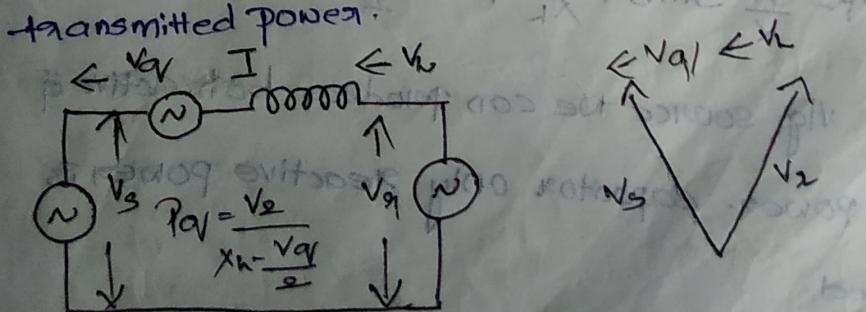thus the series capacitor compensation works by increasing the V_{lg} across the impedance of the given line, which in turn increases corresponding current I transmitted power.



Base two machine system with synchronous V_{lg} replacing the series capacitor

the steady state power transmission is same if it is transferred by series compensation provided by a synchronous Vg ac voltage source, where o/p polarity matches the voltage of series capacitor.

$$I \cdot c \quad V_g = V_c = -j X_c I = -j K X I$$

Injected compensating voltage phase

I-line current

~~$X_C \rightarrow$ reactance of series capacitor.~~

~~X - line reactance~~

~~$K = \frac{X_C}{X_L}$ degree of series compensation.~~

$$j = \sqrt{-1}$$

thus by making o/p voltage of synchronous Vg source a function of line current some compensation will be provided as a series capacitor.


the series reactive compensation scheme using a switching power converter (Voltage source converter)

As a synchronous Vg source to produce controllable Vg in quadrature with line current. this termed as static synchronous Series compensator transmitted Power is

$$P = \frac{V^2}{X} \sin \theta + \frac{V}{X_L} V \cos \frac{\theta}{2}$$

By using Vg source we can produce both active & reactive power. capacitor only reactive power is increased.

Characteristics:-

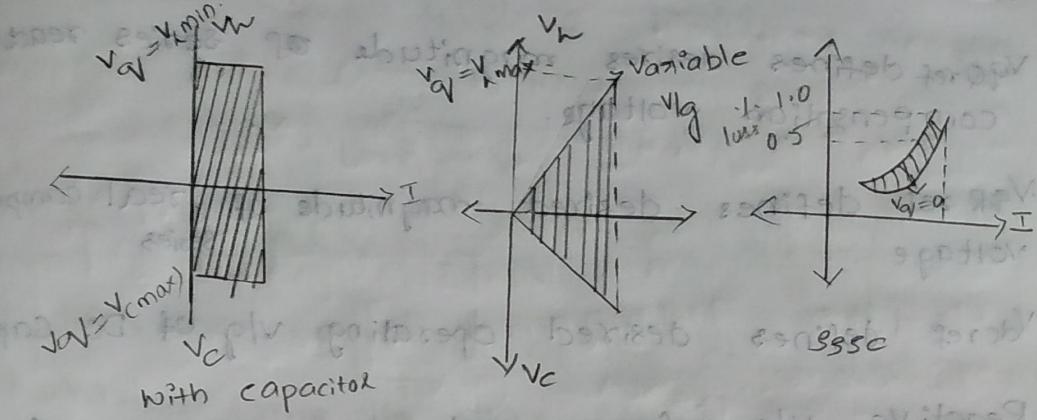

Explain SSSC & TCSC

Static synchronous series compensator (SSSC):




Definition:

The function of series capacitor is to produce an appropriate V_{lg} at the fundamental ac system frequency in quadrature with transmission line current in order to increase the V_{lg} across the inductive line impedance & thereby increase the line current & transmitter power.

The V_{lg} source converter based shunt compensator is STATcom.

The V_{lg} source converter based series compensator is SSSC.

Control Scheme of SSSC:-

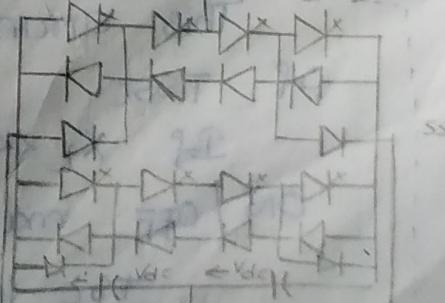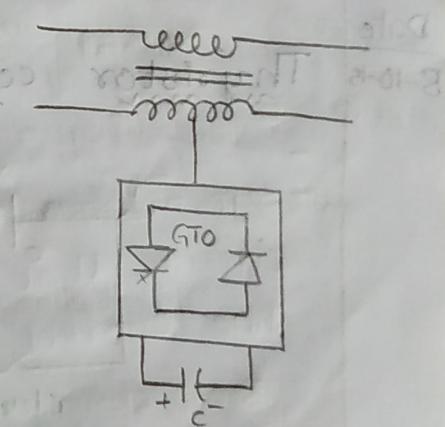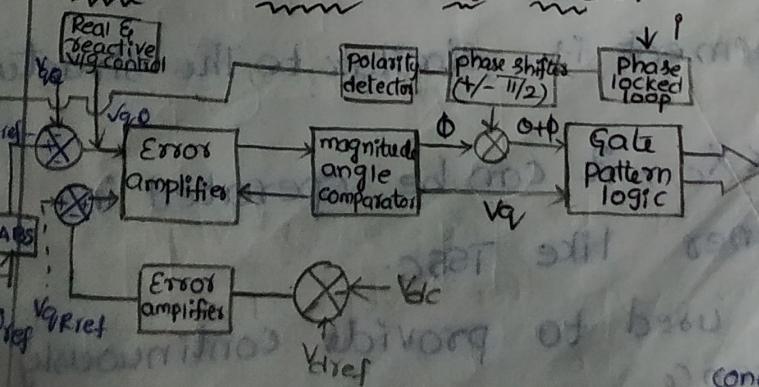

Connected in parallel to eliminate harmonics

The control is operated from $V_{Q\text{ref}}$, $V_{R\text{ref}}$, $V_{dc\text{ref}}$

$V_{Q\text{ref}}$ defines desired magnitude of series reactive compensation voltage.

$V_{R\text{ref}}$ defines desired magnitude of real compensation voltage.

$V_{dc\text{ref}}$ defines desired operating v/g of DC capacitor.


Reactive v/g reference and real voltage reference determines the real power between N_{dc} & V_g .

Magnitude of V_g & $\theta + \pi$ are used to generate gate drive signal for converter. ($V_g = V_{Qg} + V_{Rg}$)

(+ reactive power leading)
- real power lagging)

V_g - synchronous voltage source in phase quadrature with the line current improves v/g across the line.

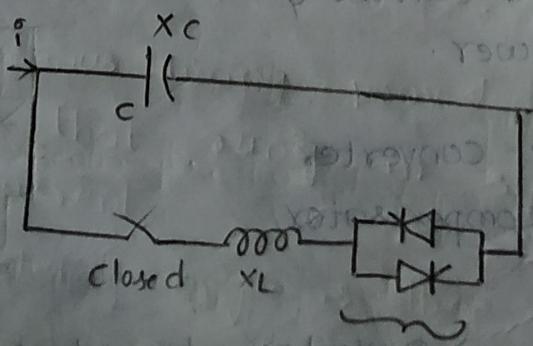Thyristor controlled Series capacitor (TCSC):



It consists of a series compensating capacitor.