

UNIT-VIII

objectives of UPFC

①

Dual converter

Unified power flow controller (UPFC)

Shunt series static var source (V_q, P_q)

Reversal of power flow possible


Def:

UPFC is a generalised synchronous vlg source represented at the fundamental frequency

by vlg phasor V_{PQ} with controllable magnitude ($0 \leq V_{PQ} \leq V_{PQ, \max}$) and

angle δ ($0 \leq \delta \leq 2\pi$) in series with transmission line

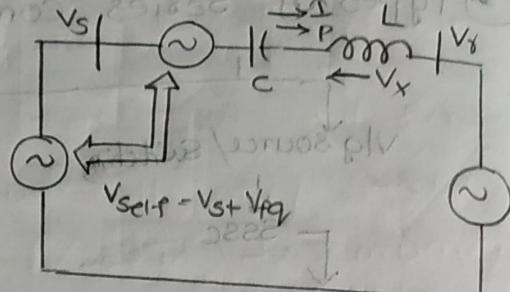Basic operating principle control structure independent real & reactive power control.




UPFC in a two machine system

(position)

Transmission line

UPFC ~ Shunt-series
↓
AC-AC converter
AC vlg controller
Cyclo Converter
Matrix converter

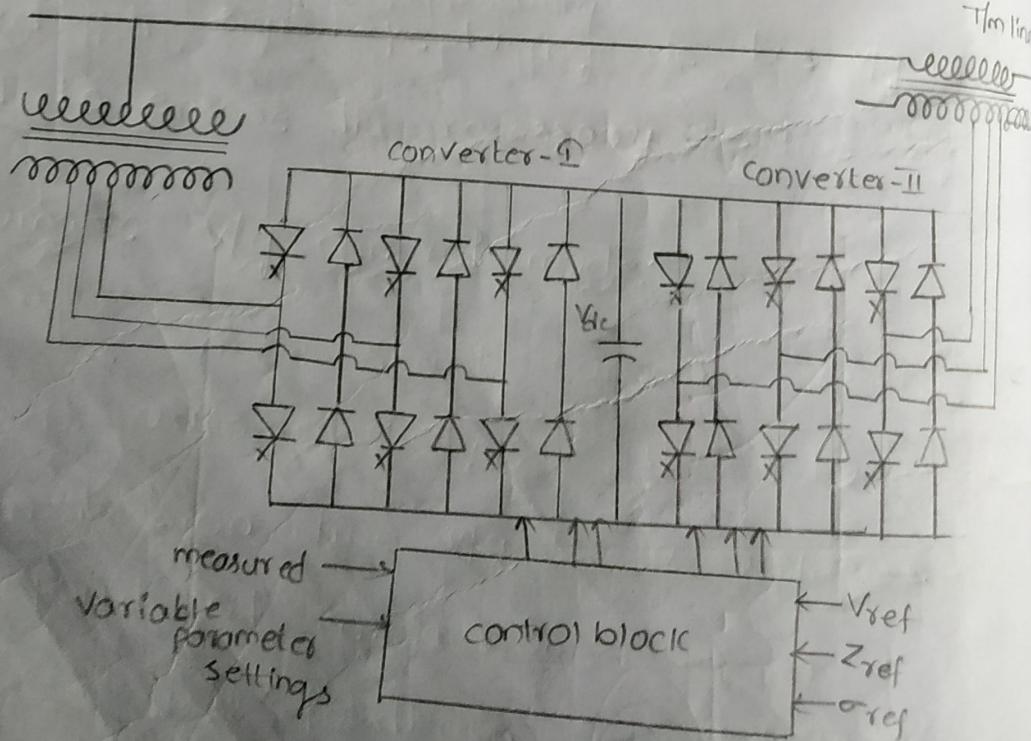JNP
um Basic function of UPFC:- (Operating principle of UPFC)



(2)

UPFC consists of V/LG source converters namely converter I and converter II operated from common DC link provided by DC storage capacitor.

- These arrangement functions as AC to AC power conversion in which real power flows in either directions. b/w ac terminals of two converters and each converter generate or absorb reactive power at ac o/p terminals.

- Basic function of converter-I is to supply (or) absorb the real power demand at converter-II. The common DC link to support real power exchange resulting from series V/LG injection.

- converter-II provides main function of UPFC by injecting a V/LG V_{PQ} controllable in magnitude & phase angle in series with the line. These injected V/LG acts as a synchronous V/LG source.


- If the transmission line current flows through the V/LG source resulting real power & reactive power exchange b/w transmission line and AC system.

Converter-I acts as a shunt controller for real power flow control.

Converter-II acts as a series controller for reactive power flow control.

- Converter-I can be operated at unity P.F for more reactive power exchange at Converter-II.

Control Structure of UPFC:-

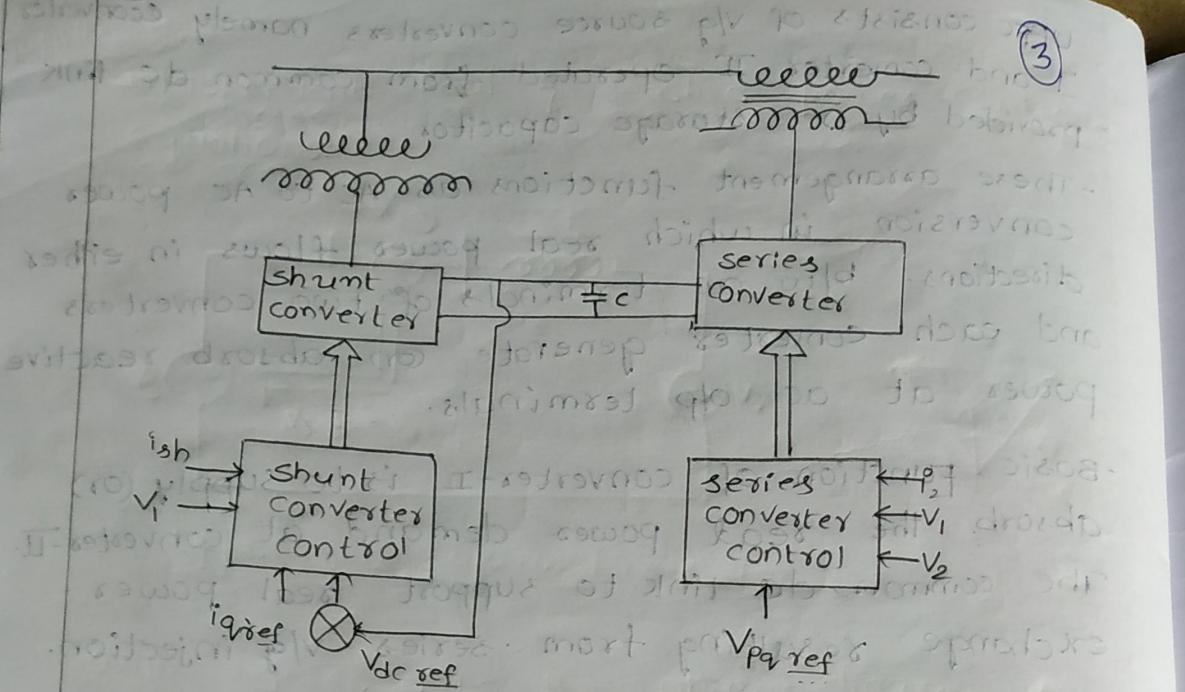

$V_1 = \text{Bus 1 P.v/g}$, $V_2 = \text{Bus 2 P.v/g}$, $V_{PQ} = V_1 + V_2$

Functional scheme of the shunt converter:

The shunt converter is operated so as to draw controlled current i_{sh} from the line.

(i) Reactive power control mode:

In this mode reference i/p is inductive (or) capacitive VAR.

A feedback signal representing replacing dc bus v/g at c is used to ensure the necessary dc line vlg.

(ii) Automatic v/g control mode:

In this mode shunt converter reactive current is automatically regulated to maintain the transmission line vlg to a reference value of the point of connection.

It uses feedback signals usually representing magnitude of positive sequence component of bus vlg v_i .

Functional control of series converter. (4)
The series converter controls the magnitude angle of the injected V_{lg} in series with the line.

i) Direct V_{lg} injection mode:-

Injected $V_{lg} V_{pq}$ is kept in phase with the system V_{lg} for V_{lg} magnitude control & in quadrature with line current I_2 provides reactive power compensation.

ii) Bus V_{lg} regulation & control mode:-

Injected $V_{lg} V_{pq}$ is kept in phase with the ilp $V_{lg} V_1$ & its magnitude controlled to maintain the magnitude of bus V_2 at the reference value.

iii) Line Impedance compensation mode:-

The magnitude of injected V_{lg} is proportional to magnitude of line current. ($V_{pq} = I_2$)

The desired impedance is specified by reference ilp and it may be complex impedance of resistive or reactive with either polarity.



iv) Phase angle regulation mode:-

The injected bus V_{lg} is controlled w.r.t ilp bus $V_{lg} V_1$ so that o/p bus $V_{lg} V_2$ is phase-shifted without any magnitude change.

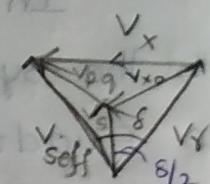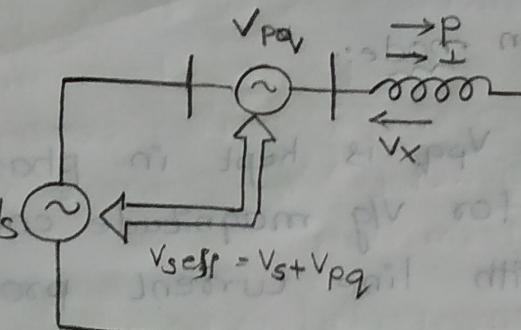v) Automatic power control mode:-

The series injected V_{lg} is determined automatically & continuously by closed loop control system to ensure that desired P & Q maintained w.r.t power changes.

Independent Real & reactive power controller
Equations:- (Q) (power angle curves) to solve



UPFC is a two machine system

V_{eff} = Sending effective voltage.

With reference to the phasor diagram the transmitted power P and the reactive power jQ_r supplied by the receiving end can be expressed as

$$P - jQ_r = V_r \left[\frac{V_s + V_{pq} - V_r}{jX} \right]^* = V_r^* \quad (1)$$

where X = conjugate of a complex number,
 $j = e^{j\pi/2} = \sqrt{-1}$

$V_{pq} = 0$ then describes the uncompensated line

$$P - jQ = V_r \left[\frac{V_s - V_r}{jX} \right]^* \sim \text{Real power}$$

Thus when $V_{pq} \neq 0$ the total real & reactive Power can be expressed as

$$P - jQ_r = V_r \left[\frac{V_s - V_r}{jX} \right]^* + \frac{V_r V_{pq}}{-jX}^*$$

Substituting $V_s = V e^{j\delta/2}$

$$= V \left(\cos \frac{\delta}{2} + j \sin \frac{\delta}{2} \right)$$

$$V_r = V e^{-j\delta/2}$$

$$= V \left(\cos \frac{\delta}{2} - j \sin \frac{\delta}{2} \right)$$

$$V_p = V \left(\cos \frac{\delta}{2} - j \sin \frac{\delta}{2} \right) \quad (6)$$

$$V_{pq} = V_{pq} e^{j(\frac{\delta}{2} + \delta_0)}$$

$$= V_{pq} \left[\cos \left(\frac{\delta}{2} + \delta_0 \right) + j \sin \left(\frac{\delta}{2} + \delta_0 \right) \right]$$

$$P[\delta_0, \delta] = P_0(\delta) + P_{pq}(\delta)$$

$$P[\delta_0, \delta] = \frac{V^2}{X} \sin \delta - \frac{V V_{pq}}{X} \cos \left(\frac{\delta}{2} + \delta_0 \right) \sim \text{real power}$$

$$Q[\delta_0, \delta] = Q_0(\delta) + Q_{pq}(\delta)$$

$$Q[\delta_0, \delta] = \frac{V^2}{X} (1 - \cos \delta) - \frac{V V_{pq}}{X} \sin \left(\frac{\delta}{2} + \delta_0 \right) \sim \text{reactive power}$$

